

tain a reduction in ripple voltage adequate for many purposes simply by supplying filtered d.c. to the screens with a consequent saving in weight and cost. The accompanying table shows the performance of the circuit of Fig. 12-23. Column I shows various output voltages, while Column II shows the maximum current that can be drawn at that voltage with negligible variation in output voltage. Column III shows the measured ripple at the maximum current. The second part of the table shows the variation in ripple with load current at 300 volts output.

### High-Voltage Regulators

Regulated screen voltage is required for screen-grid tubes used as linear amplifiers in single-side-band operation. Figs. 12-24 through 12-27 show various different circuits for supplying regulated voltages up to 1200 volts or more.

In the circuit of Fig. 12-24, gas-filled regulator tubes are used to establish a fixed reference voltage to which is added an electronically regulated variable voltage. The design can be modified to give any voltage from 225 volts to 1200 volts, with each design-center voltage variable by plus or minus 60 volts.

The output voltage will depend upon the number and voltage ratings of the VR tubes in the string between the 991 and ground. The total VR-tube voltage rating needed can be determined by subtracting 250 volts from the desired output voltage. As examples, if the desired output voltage is 350, the total VR-tube voltage rating should be  $350 - 250 = 100$  volts. In this case, a VR-105 would be used. For an output voltage of 1200, the VR-tube voltage rating should be

Table of Performance for Circuit of Fig. 12-23

I	II	III	Output voltage — 300	
450 v.	22 ma.	3 mv.	150 ma.	2.3 mv.
425 v.	45 ma.	4 mv.	125 ma.	2.8 mv.
400 v.	72 ma.	6 mv.	100 ma.	2.6 mv.
375 v.	97 ma.	8 mv.	75 ma.	2.5 mv.
350 v.	122 ma.	9.5 mv.	50 ma.	3.0 mv.
325 v.	150 ma.	3 mv.	25 ma.	3.0 mv.
300 v.	150 ma.	2.3 mv.	10 ma.	2.5 mv.

$1000 - 250 = 750$  volts. In this case, five VR-150s would be used in series.

The maximum voltage output that can be obtained is approximately equal to 0.7 times the r.m.s. voltage of the transformer  $T_1$ . The current rating of the transformer must be somewhat above the load current to take care of the voltage dividers and bleeder resistances.

A single 6L6 will handle 90 ma. For larger currents, 6L6s may be added in parallel.

The heater circuit supplying the 6L6 and 6SJ7 should *not* be grounded. The shaft of  $R_1$  should be grounded. When the output voltage is above 300 or 400, the potentiometer should be provided with an insulating mounting, and should be controlled from the panel by an extension shaft with an insulated coupling and grounded control.

In some cases where the plate transformer has sufficient current-handling capacity, it may be desirable to operate a screen regulator from the plate supply, rather than from a separate supply. This can be done if a regulator tube is used that can take the required voltage drop. In Fig. 12-25, a type 211 or 812A is used, the control tube being a 6AQ5. With an input voltage of 1800 to 2000, an output voltage of 500 to 700 can be

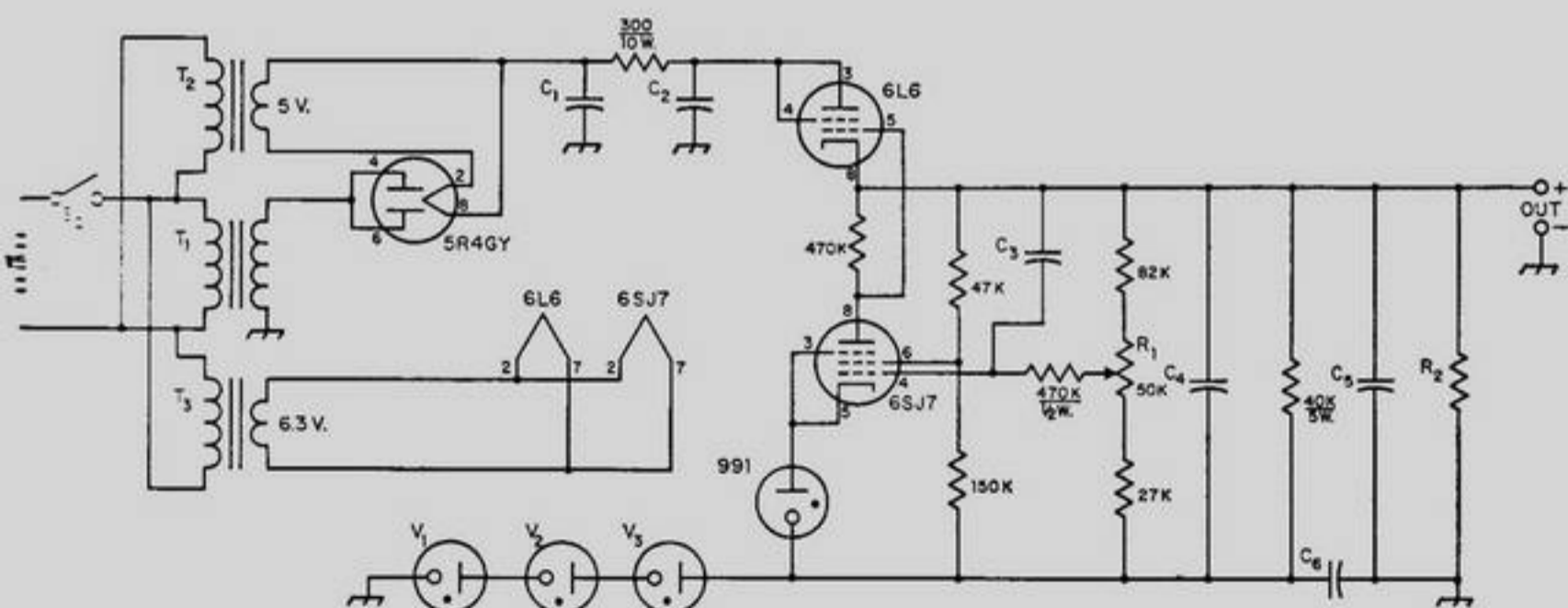


Fig. 12-24—High-voltage regulator circuit by W4PRM. Resistors are 1 watt unless indicated otherwise.

$C_1$ —4- $\mu$ f. paper, voltage rating above peak-voltage output of  $T_1$ .

$C_2$ —0.1- $\mu$ f. paper, 600 volts.

$C_3$ —12- $\mu$ f. electrolytic, 450 volts.

$C_4$ —40- $\mu$ f., voltage rating above d.c. output voltage.

Can be made up of a combination of electrolytics in series, with equalizing resistor. (See section on ratings of filter components.)

$C_5$ —4- $\mu$ f. paper, voltage rating above voltage rating of VR string.

$R_1$ —50,000-ohm, 4-watt potentiometer.

$R_2$ —Bleeder resistor, 50,000 to 100,000 ohms, 25 watts (not needed if equalizing resistors mentioned above are used).

$T_1$ —See text.

$T_2$ —Filament transformer; 5 volts, 2 amp.

$T_3$ —Filament transformer; 6.3 volts, 1.2 amp.

$V_1$ ,  $V_2$ ,  $V_3$ —See text.